

Lab 6 Report

Avron Phan, utp2323


Aneer Patel, aap4484

a) HCM Design

• Goals



- reuse old code to reduce complexity
- modify as needed
- make sure clock freq is fast enough to "simultaneously" display all 10 numbers (in reality, its switching between all 10 numbers at a high rate)
- Modified previous time mux module to act as controller FSM
- Reused clock divider with 10 ms freq
- Reused hex \rightarrow 7 seg for conversion to display

Pseudo Code Flowchart

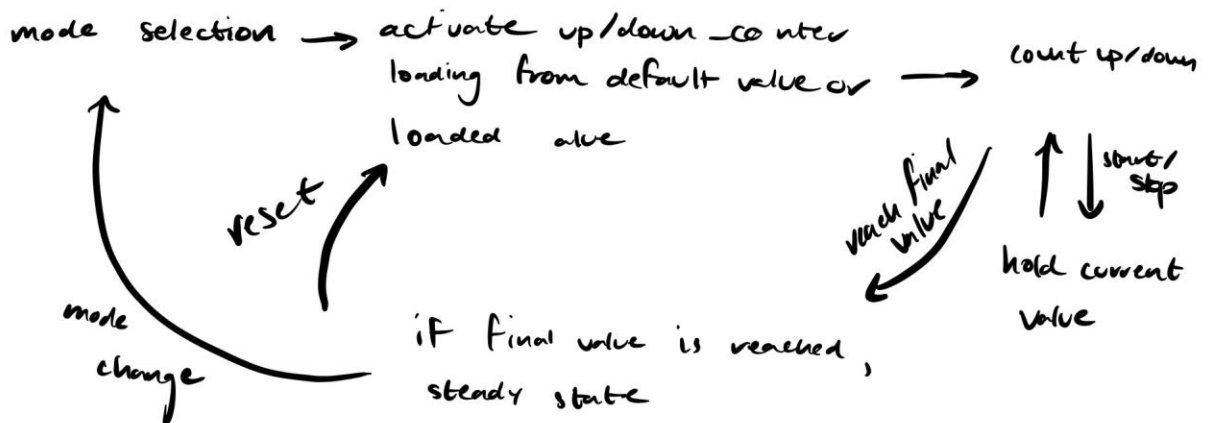

- Segment changing functions like RCT; if the right-most seg is a, it generates a carry-in, which accordingly generates carry-ins if necessary, and sets corresponding segs to 0.


b) Processor Design

 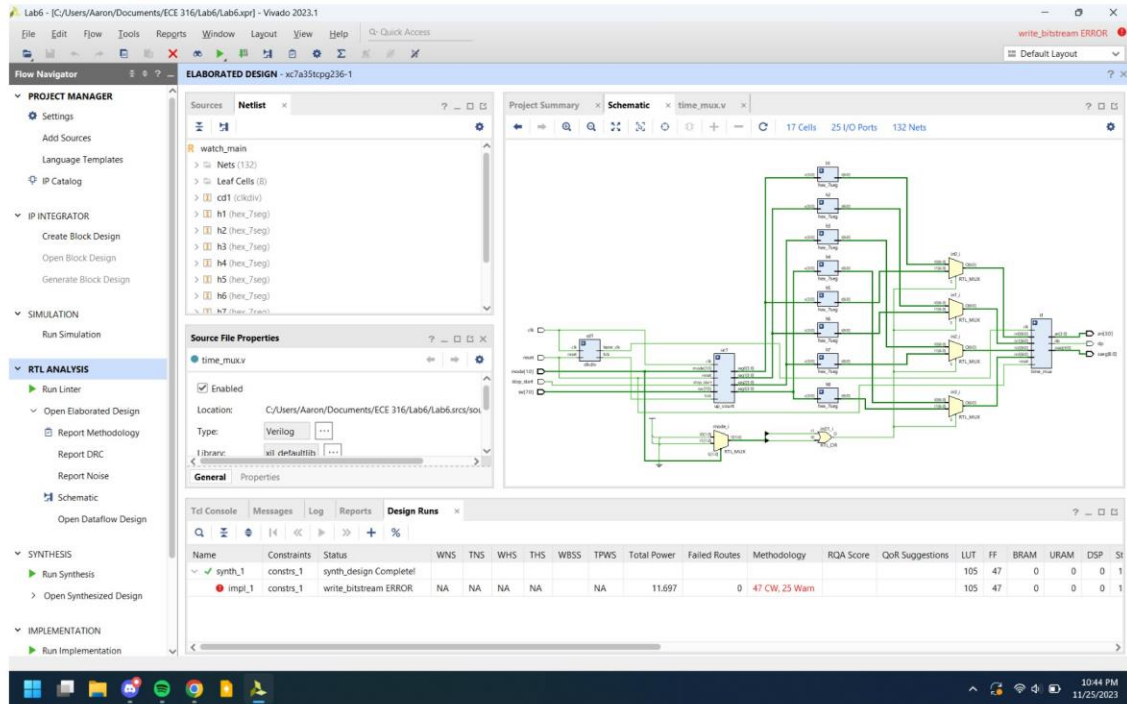

mode 0 = 0, 00.00
 mode 1 = 1, xx.00
 mode 2 = 2, 99.99
 mode 3 = 3, xx.00

• time m x FSM

* rising edge change

 

Watch Main:

```
module watch_main(
    input clk,
    input reset,
    input [7:0] sw,
    input [1:0] mode,
    output [3:0] an,
    output [6:0] sseg,
    output dp,
    input stop_start
);

    localparam [6:0] zero = 7'b0000001;

    wire[6:0] in0, in1, in2, in3;
    wire[6:0] iu0, iu1, iu2, iu3;
    wire[6:0] id0, id1, id2, id3;
    wire[3:0] su0, su1, su2, su3;
    wire[3:0] sd0, sd1, sd2, sd3;
    wire tick;
    wire slow_clk, faster_clk;

    clkdiv cd1(.clk(clk), .reset(reset), .slow_clk(slow_clk), .tick(tick), .faster_clk(faster_clk));
    up_count uc1(.clk(clk), .reset(reset), .tick(tick), .stop_start(stop_start), .mode(mode), .sw(sw),
    .seg0(su0), .seg1(su1), .seg2(su2), .seg3(su3));
    //down_count dc1();    //to be implemented

    hex_7seg h1(.x(su0), .r(id0));
    hex_7seg h2(.x(su1), .r(id1));
```

```
hex_7seg h3(.x(su2), .r(id2));
```

```
hex_7seg h4(.x(su3), .r(id3));
```

```
hex_7seg h5(.x(su0), .r(iu0));
```

```
hex_7seg h6(.x(su1), .r(iu1));
```

```
hex_7seg h7(.x(su2), .r(iu2));
```

```
hex_7seg h8(.x(su3), .r(iu3));
```

```
assign in0 = ((mode == 2'b00 || mode == 2'b01)?id0:iu0);
```

```
assign in1 = ((mode == 2'b00 || mode == 2'b01)?id1:iu1);
```

```
assign in2 = ((mode == 2'b00 || mode == 2'b01)?id2:iu2);
```

```
assign in3 = ((mode == 2'b00 || mode == 2'b01)?id3:iu3);
```

```
time_mux t1(.clk(faster_clk), .reset(reset), .in0(in0), .in1(in1), .in2(in2), .in3(in3), .sseg(sseg), .an(an),  
.dp(dp));
```

```
endmodule
```

Clock Divider

```
module clkdiv(
```

```
    input clk,
```

```
    input reset,
```

```
    output slow_clk,
```

```
    output faster_clk,
```

```
    output tick
```

```
);
```

```
reg[19:0] COUNT;
```

```
assign faster_clk = COUNT[14];
```

```
assign slow_clk = COUNT[19];
```

```

always @(posedge clk or posedge reset)
begin
    if(reset)
        begin
            COUNT <= 0;
        end
    else
        COUNT <= COUNT + 1;
    end

    assign tick = ((COUNT == 1000000)?1'b1:1'b0);
endmodule

```

Up/Down Count Logic

```

module up_count(
    input clk,
    input reset,
    input tick,
    input stop_start,
    input [1:0] mode,
    input [7:0] sw,
    output reg[3:0] seg0,
    output reg[3:0] seg1,
    output reg[3:0] seg2,
    output reg[3:0] seg3
);

```

```

    reg stop = 0;

```

```

always@(posedge clk or posedge reset)

```

```

begin
    if(reset)    //if reset button is pressed,
        begin
            case(mode)

                2'b00:begin    //mode 1, count up from 0
                    seg0<=0;
                    seg1<=0;
                    seg2<=0;
                    seg3<=0;
                    stop<=0;
                end

                2'b01: begin    //mode 2, count up from loaded val
                    seg0<=0;
                    seg1<=0;
                    seg2<=sw[3:0];    //second digit of seconds
                    seg3<=sw[7:4];    //first digit of seconds
                    stop<=0;
                end

                3'b10: begin
                    seg0<=9;
                    seg1<=9;
                    seg2<=9;
                    seg3<=9;
                    stop<=0;
                end
            endcase
        end
    end

```

```

2'b11: begin    //mode 2, count up from loaded val
seg0<=0;
seg1<=0;
seg2<=sw[3:0];    //second digit of seconds
seg3<=sw[7:4];    //first digit of seconds
stop<=0;
end

default: stop<=0;
endcase
end

else if(stop_start)    //if the stop/start button is pressed
begin    //retain current value
if(stop == 0)
stop<=1;
else if(stop == 1)
stop<=0;
end
else if((tick && stop) &&(mode == 0 || mode==1))
begin
if(seg0==9)
begin
if(seg3==9 && seg2==9 && seg1 == 9) //all segments equal to max
seg0<=0;
else
seg0<=0;
if(seg1==9)
begin

```

```

if(seg3==9 && seg2==9)
    seg1<=9;
else
    seg1<=0;
    if(seg2==9 && seg3!=9)
        begin
            seg2<=0;
            if(seg3>=9)
                seg3=9;
            else if(seg3!=9)
                seg3<=seg3+1;
            end
            else if(seg2!=9)
                seg2<=seg2+1;
            end
            else if(seg1!=9)
                seg1<=seg1+1;
            end
        else if(seg0!=9)
            seg0<=seg0+1;
        end
        else if ((tick && stop) && (mode == 2 || mode==3))
            begin
                if (seg0 == 0) // if seg0 reaches 0, decrement other segments
                    begin
                        if (seg1 == 0)
                            begin
                                if (seg2 == 0)
                                    begin

```



```

        if (seg3 == 0)
            stop <= 1; // Stop counting when all segments reach 0
        else
            seg3 <= seg3 - 1;
        end
    else
        seg2 <= seg2 - 1;
    end
else
    seg1 <= seg1 - 1;
    seg0 <= 9;
end
else
    seg0 <= seg0 - 1;
end
end
end
endmodule

```

Hex-to-7 segment decoder

```

module hex_7seg(
    input[3:0]x,
    output reg[6:0]r
);
    always@(*)
        case(x)
            4'b0000 : r = 7'b0000001;
            4'b0001 : r = 7'b1001111;
            4'b0010 : r = 7'b0010010;
            4'b0011 : r = 7'b0000110;
            4'b0100 : r = 7'b1001100;

```

```

        4'b0101 : r = 7'b0100100;
        4'b0110 : r = 7'b0100000;
        4'b0111 : r = 7'b0001111;
        4'b1000 : r = 7'b0000000;
        4'b1001 : r = 7'b0000100;
        4'b1010 : r = 7'b0001000;
        4'b1011 : r = 7'b1100000;
        4'b1100 : r = 7'b0110001;
        4'b1101 : r = 7'b1000010;
        4'b1110 : r = 7'b0110000;
        4'b1111 : r = 7'b0111000;
    endcase
endmodule

```

Time Multiplexer (FSM Controller)

```

module time_mux(
    input clk,
    input reset,
    input [6:0] in0,
    input [6:0] in1,
    input [6:0] in2,
    input [6:0] in3,
    output reg[6:0] sseg,
    output reg[3:0] an,
    output reg dp
);

    reg[1:0] state;
    reg[1:0] next_state;

```

```
localparam [6:0] zero = 7'b0000001;
```

```
localparam [6:0] nine = 7'b0001100;
```

```
always@(*)begin
```

```
    case(state)
```

```
        2'b00: next_state = 2'b01;
```

```
        2'b01: next_state = 2'b10;
```

```
        2'b10: next_state = 2'b11;
```

```
        2'b11: next_state = 2'b00;
```

```
    endcase
```

```
end
```

```
always@(*)begin
```

```
    case(state)
```

```
        2'b00: sseg = in0;
```

```
        2'b01: sseg = in1;
```

```
        2'b10: sseg = in2;
```

```
        2'b11: sseg = in3;
```

```
    endcase
```

```
case(state)
```

```
    2'b00:
```

```
        begin
```

```
            an = 4'b1110;
```

```
            dp = 1'b1;
```

```
        end
```

```
    2'b01:
```

```
        begin
```

```
            an = 4'b1101;
```

```
        dp = 1'b1;
    end
    2'b10:
        begin
            an = 4'b1011;
            dp = 1'b0;
        end
    2'b11:
        begin
            an = 4'b0111;
            dp = 1'b1;
        end
    endcase
end
```

```
always@(posedge clk or posedge reset)
begin
    if(reset)
        begin
            state<=2'b00;
        end
    else
        state<=next_state;
    end
endmodule
```